



ON Semiconductor

Utilizing GaN HEMTs in an All-in-One Workstation Power Supply

Introduction

The all-in-one workstation is getting sleeker and lighter with every new model. One of the key enablers to this trend is lighter and small form-factor power converter which is typically achieved by switching the power converter at a high frequency. High frequency switching leads to smaller and lighter passive components such as transformers, inductors and capacitors. A key impediment for high switching frequency operation is the switching & driving losses of the traditional silicon MOSFETs. **GaN HEMTs** (Gallium Nitride –High Electron Mobility Transistor) offer low gate charge and on-resistance compared to the traditional MOSFETs enabling high frequency power conversion. *GaN HEMTs switch very fast and the resulting dv/dt is high. Therefore, it requires special probing techniques that are highlighted towards the end of this application note.*

This application note describes the performance of a 12 V/20 A all-in-one computer power supply using GaN HEMTs as the switching devices. The front-end of the power converter converts a universal AC line to a 385 DC bus while achieving near unity power factor. The second stage is a DC-DC stage that converts the 385 V DC bus to a 12 V output with a max rated load current of 20 A.

Power Converter Specifications

The demo board has been designed as a universal input 240 watt board. It produces a 12 volt dc output voltage, at up to 20 A load current. The power factor is greater than 98% at low line and the T.H.D is less than 17% at full load. Table 1 list out all the specifications.

| Requirement | Min. | Max. | Unit |
|---------------------|------|------|------|
| Input Voltage (ac) | 90 | 265 | V |
| Output Voltage (dc) | - | 12 | V |
| Output Current(dc) | 0 | 20 | A |
| Output Power | 0 | 240 | W |
| Power Factor | - | >98 | % |

Table 1 Demo Board Specifications

Overview of the Architecture

An overview of the architecture is shown in the Figure 1 below. The front- end converts the AC into a regulated 385 V DC bus. This is achieved using a power factor correction (PFC) IC employing a topology. The inductor current in the boost converter works in CCM (Continuous. Conduction Mode). The Boost PFC stage employs ON Semiconductor’s NCP1654 controller. The second stage is an isolated DC-DC converter that converts the 385 V DC bus to a 12 V dc voltage output. The isolated DC-DC conversion is achieved using a resonant topology popularly known as LLC topology. Synchronous rectifiers are used on the secondary for higher efficiency. The LLC power converter employs ON’s NCP1397 while the synchronous rectifier driver is NCP4304. The NCP432 is utilized in the feedback path to regulate the output voltage. The board utilizes GaN HEMTs from Transphorm Inc. as the switching devices in both the PFC stage and in the primary side of the LLC stage.

DN05067/D

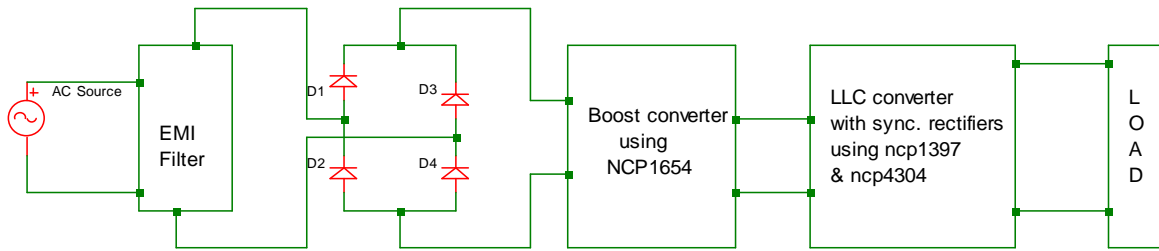


Figure1 Block Diagram of the demo board

GaN HEMTs

The demonstration board uses TPH3002PS GaN based switches from Transphorm Inc. The TPH3002PS includes a GaN HEMT and a low-voltage, low $R_{ds(on)}$ silicon FET in a cascode structure as shown in the figure. Therefore, the control terminal aka gate is that of a standard silicon FET. These devices have a low $R_{ds(on)}$, and high dv/dt . Traditional silicon has a dv/dt of less than 50V/ns while TPH3002PS has a dv/dt of >100V/ns. These factors result in low switching and conduction losses. TPH3002PS has low Q_{rr} which result in minimal reverse recovery losses. Some of the parameters of TPH3002PS are given in the table below

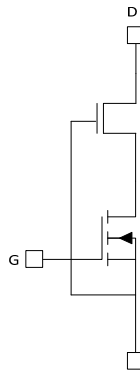


Figure 2. Cascoded GaN HEMT and Low Voltage Silicon FET

| S.No | Parameter | Value | Unit | Conditions |
|------|--------------|-------|------|--------------------------------|
| 1 | $R_{ds(on)}$ | 0.29 | mOhm | $I_d = 9$ A continuous current |
| 2 | Q_g | 6.2 | nC | |
| 3 | Q_{rr} | 29 | nC | |
| 4 | E_{oss} | 3.1 | uJ | |

Table 2 TPH3002PS parameters[6]

PFC Circuit Description

As explained earlier, the inductor current in the boost PFC is in CCM. The CCM operation results in lower peak and RMS currents compared to Critical Conduction Mode (CrM). The CrM operation brings in a number of other benefits but is typically employed at lower power levels. The CCM operation greatly simplifies the design of the boost inductor and reduces the stress on the boost FET and boost diode. Also, the CCM boost works in fixed frequency simplifying the EMI filter design. NCP1654 is a simplified CCM boost PFC converter in an 8-pin package that minimizes the number of external components. Figure 3 below show a typical application circuit of the NCP1654 based PFC [1]. Salient features NCP1654 provides are mentioned below:

1. Programmable Overcurrent Protection
2. Brownout Detection
3. Overvoltage Protection
4. Soft Start
5. Continuous Conduction Mode
6. Average Current-Mode or Peak Current-Mode Operation
7. Programmable Overpower Limitation
8. Under voltage Detection for Open Loop Detection (shutdown)
9. Inrush Currents Detection

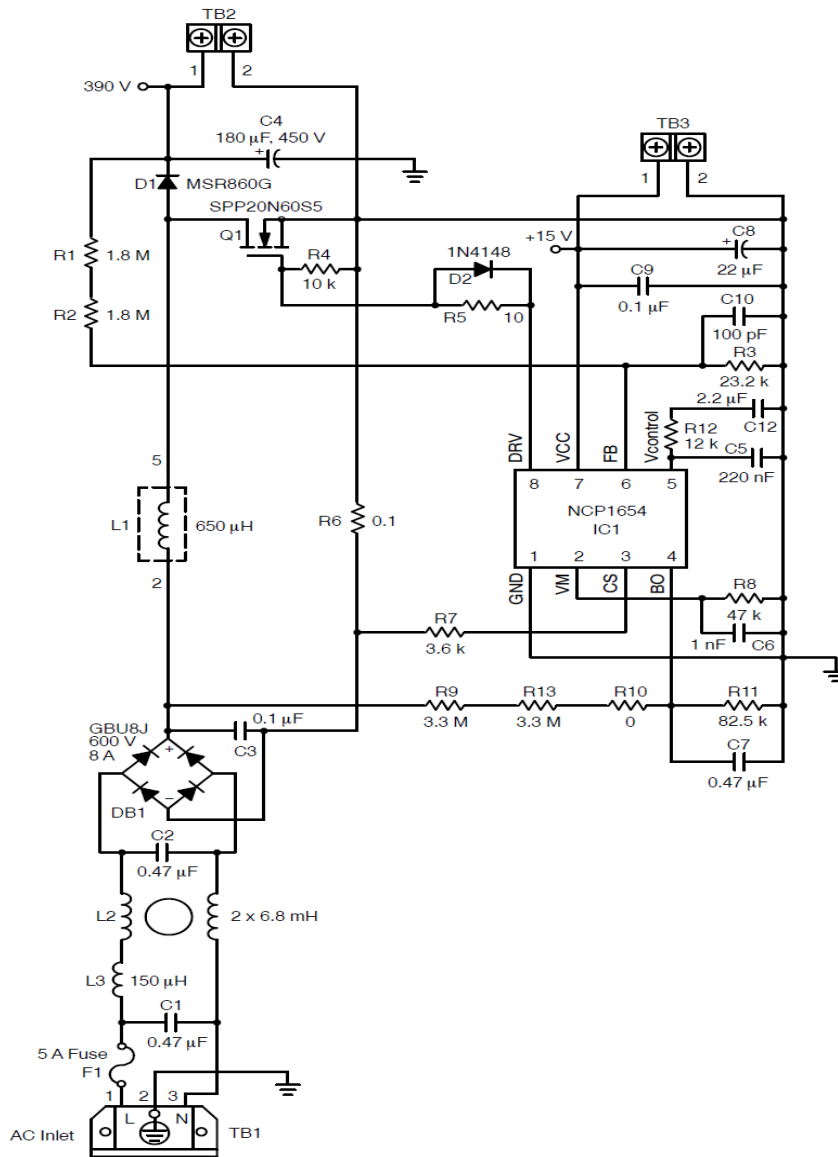


Figure 3 Typical application circuit of NCP1654 based PFC Circuit

The design table of PFC circuit is given in [6].

LLC Circuit Description

The LLC power converter is a variant of a series resonant converter. The abbreviation LLC comes from the fact that this converter utilizes two inductors ($L_{\text{Magnetizing}}$ and L_{Resonant}) and a capacitor (C) to form a resonant circuit. Typically, the leakage of the transformer acts as extra the resonant inductance in lieu of an extra discrete inductor. The LLC stage design is based on NCP1397 and NCP4304B and is explained in AND8460-D [4].

A typical application circuit of NCP1397 is shown in Figure 4[2]

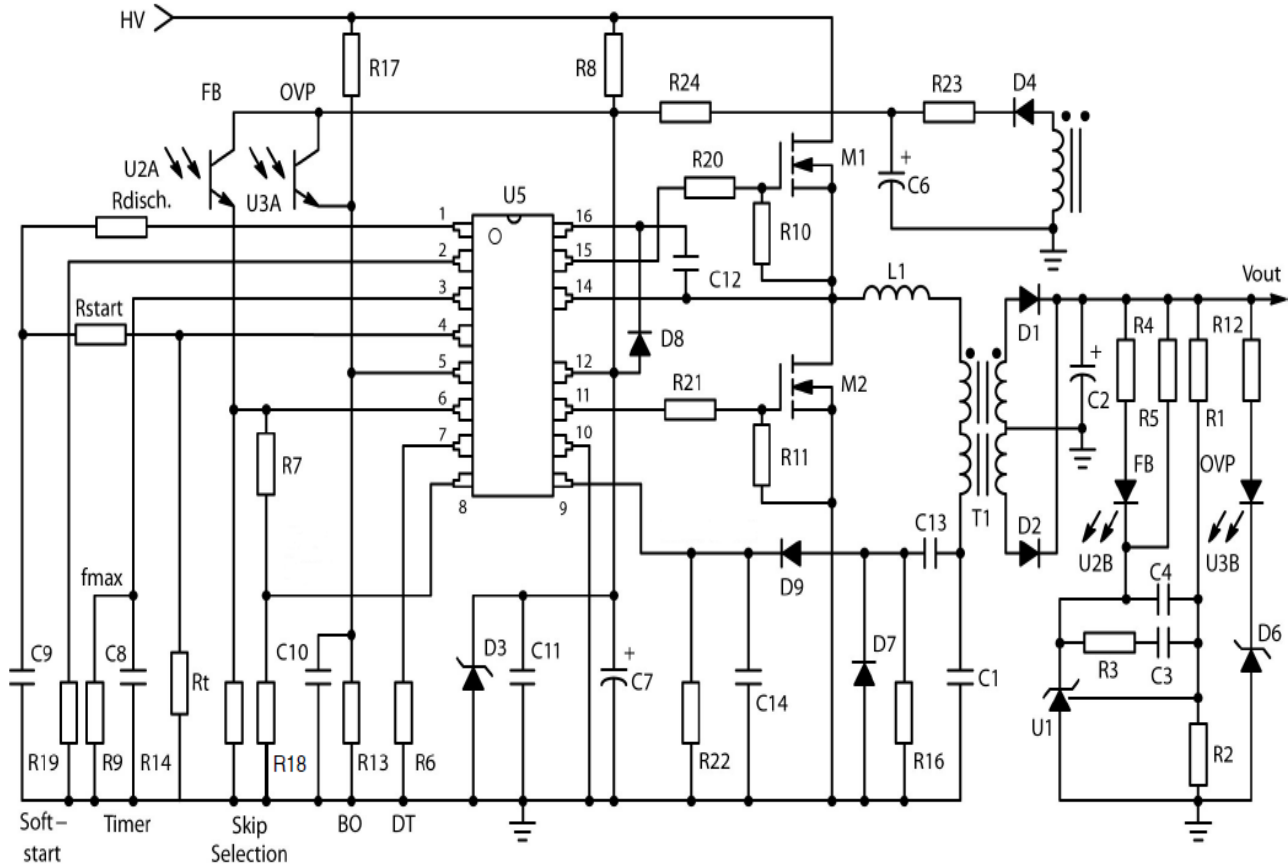


Figure 4 Typical application circuit of NCP1397

Following are the salient features of the NCP1397:

1. Adjustable minimum switching frequency with 3% accuracy
2. Brown-out input
3. 1 A / 0.5 A Peak Current Sink / Source Drive
4. Timer-based OCP input with auto-recovery
5. Second latched OCP level
6. Adjustable dead time from 100 ns to 2 us
7. Adjustable soft-start

To achieve better efficiency, synchronous rectifiers are used on the secondary of the LLC converter. The NCP4304 SR [3] controller is utilized for the control of secondary side FETs. NCP4304 is a proprietary SR controller from ON Semiconductor which provides true secondary zero current detection and automatic parasitic inductance compensation. Typical application circuit of the NCP4304 is given in Figure 5[3]. Some of its salient features are:

DN05067/D

1. Precise True Secondary Zero Current Detection with Adjustable Threshold
2. Automatic Parasitic Inductance Compensation
3. Typically 40 ns Turn off Delay from Current Sense Input to Driver
4. Zero Current Detection Pin Capability up to 200 V
5. Optional Ultrafast Trigger Input
6. Disable Input
7. Adjustable Minimum ON Time and Minimum OFF Time
8. 5 A/2.5 A Peak Current Sink/Source Drive Capability
9. Operating Voltage Range up to 30V.

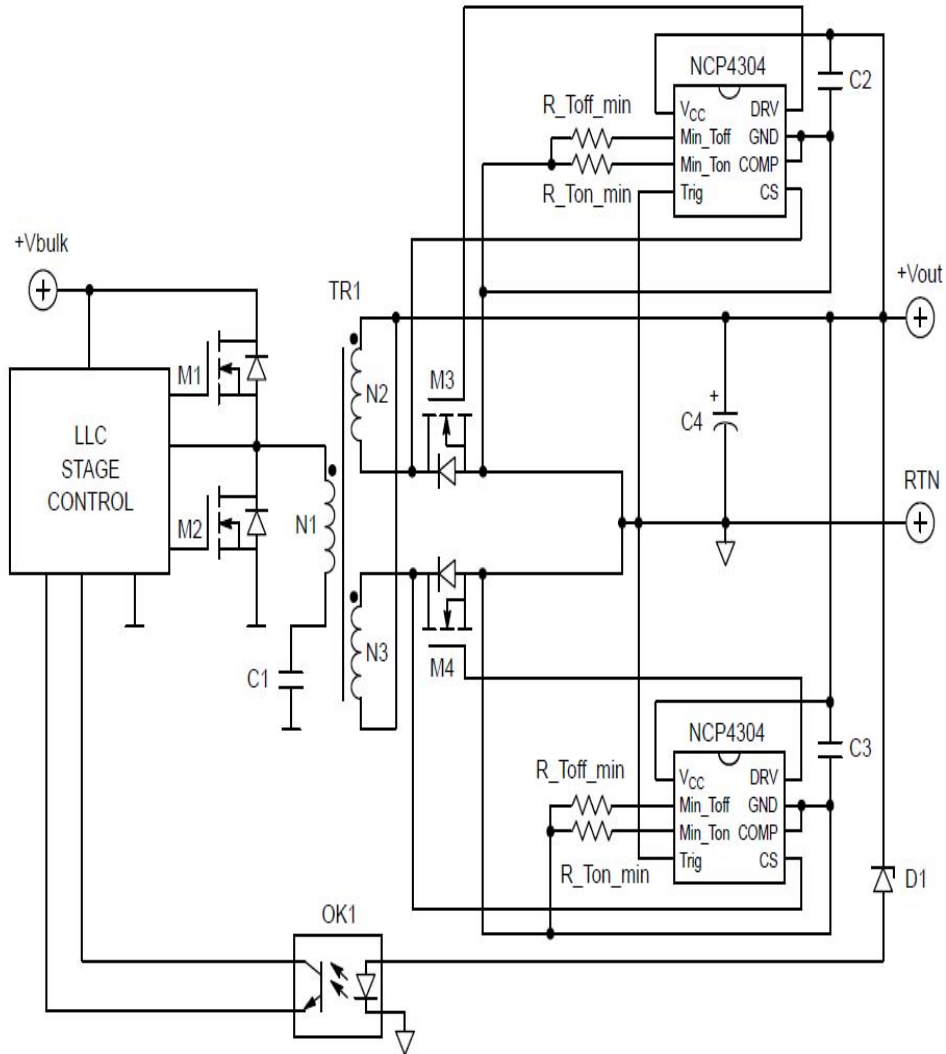


Figure 5 Typical application circuit of NCP4304B

Performance

Efficiency, Power factor and THD were measured at low line and high line input voltages. Chroma programmable AC source 61604, Chroma power meter 66202 and Chroma electronic load 63107 were used for the measurement purpose. Table 3 and 4 show the T.H.D and Power Factor data at low and high line respectively. The graphs below show the efficiency of the boost converter, LLC converter and the complete board.

P.F.C

115 Volts AC Input

| S.No | Output Voltage | Output Current | T.H.D | Power Factor |
|------|----------------|----------------|--------|--------------|
| 1 | 12.062 | 4.997 | 18.537 | 0.9705 |
| 2 | 12.053 | 9.9663 | 11.62 | 0.9837 |
| 3 | 12.06 | 14.95 | 8.8442 | 0.9877 |
| 4 | 12.04 | 19.94 | 7.8168 | 0.9892 |

Table 3 T.H.D. and Power Factor at 115 Volt 60 Hz input

230 Volts AC Input

| S.No | Output Voltage | Output Current | T.H.D | Power Factor |
|------|----------------|----------------|--------|--------------|
| 1 | 12.055 | 4.9975 | 19.936 | 0.9216 |
| 2 | 12.047 | 9.965 | 13.961 | 0.9659 |
| 3 | 12.04 | 14.953 | 13.594 | 0.9714 |
| 4 | 12.037 | 19.94 | 12.472 | 0.9737 |

Table 4 T.H.D. and Power Factor at 230 Volt 50 Hz input

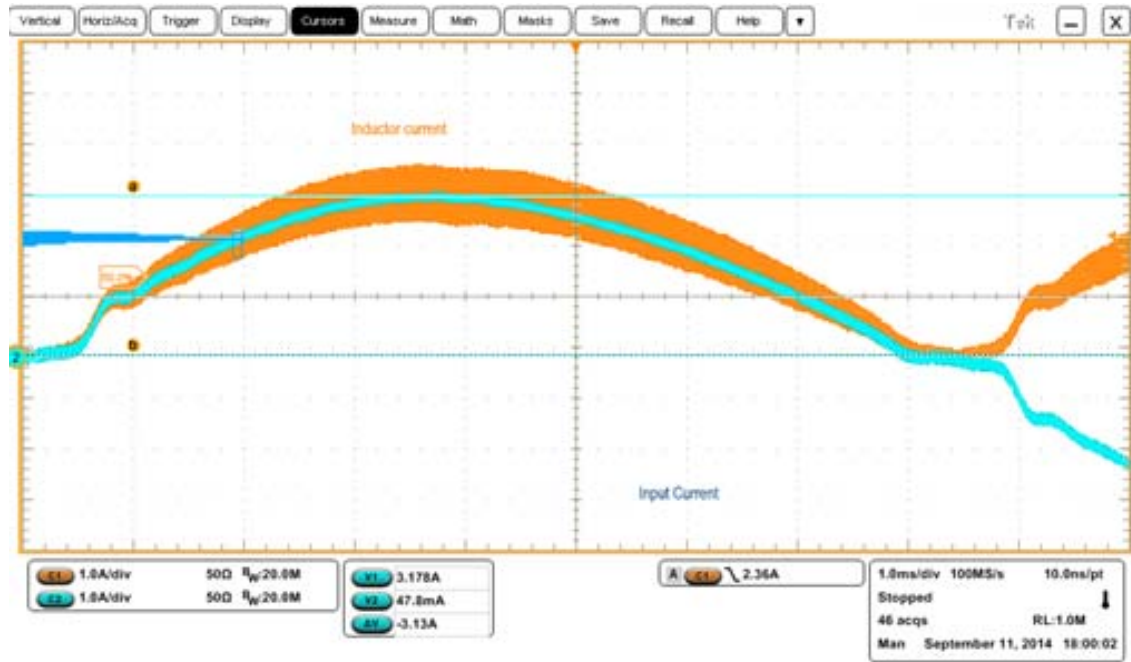


Figure 6 Inductor Current vs. Input current

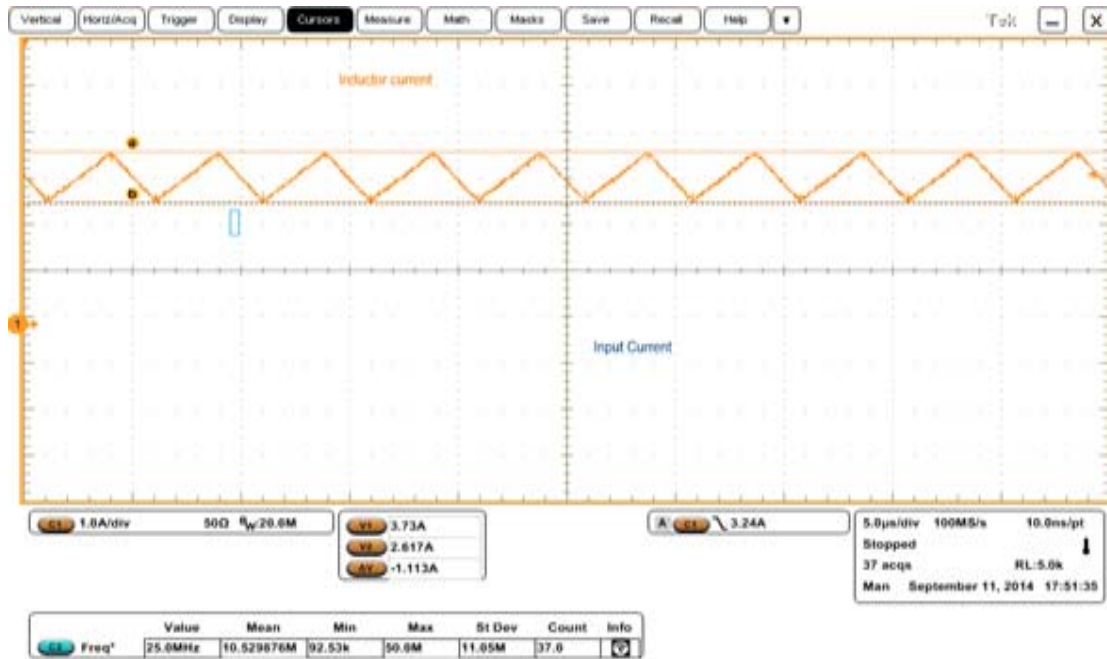


Figure 7 Inductor Current

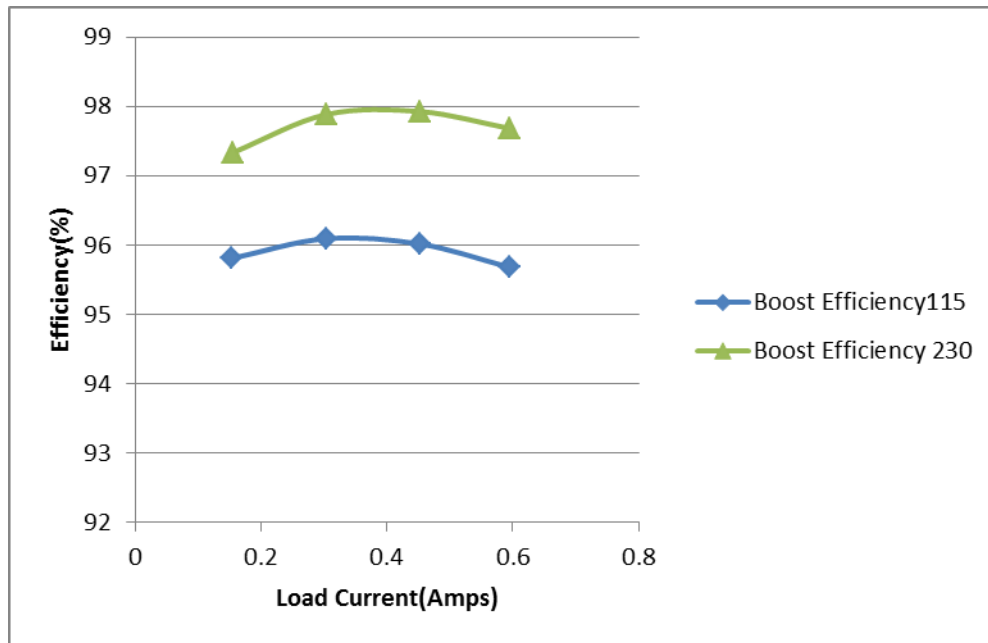


Figure 8 Boost Converter Efficiency

LLC

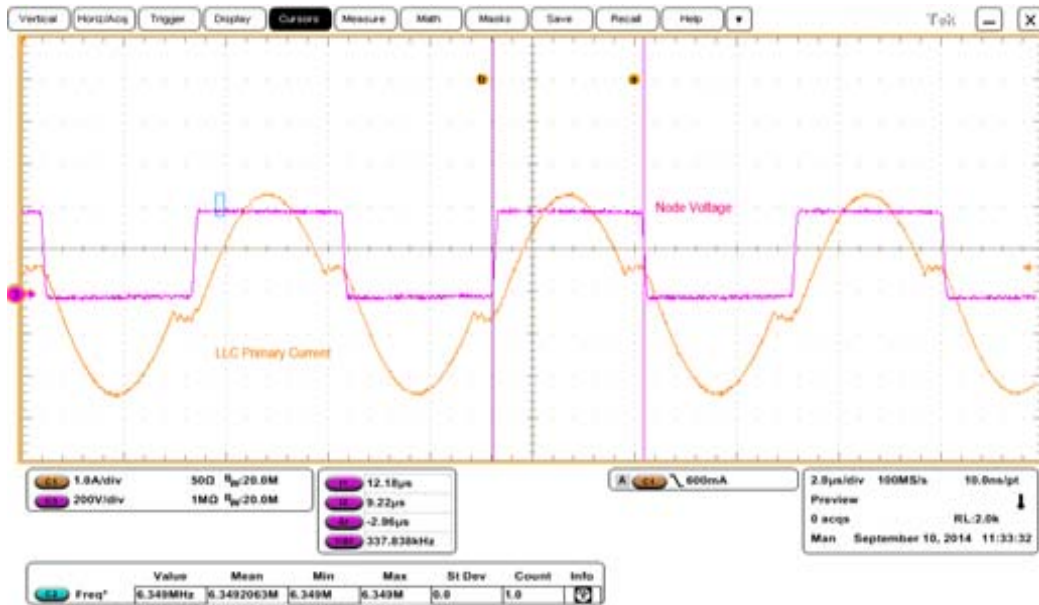


Figure 9 LLC inductor current vs node voltage (20 A load)

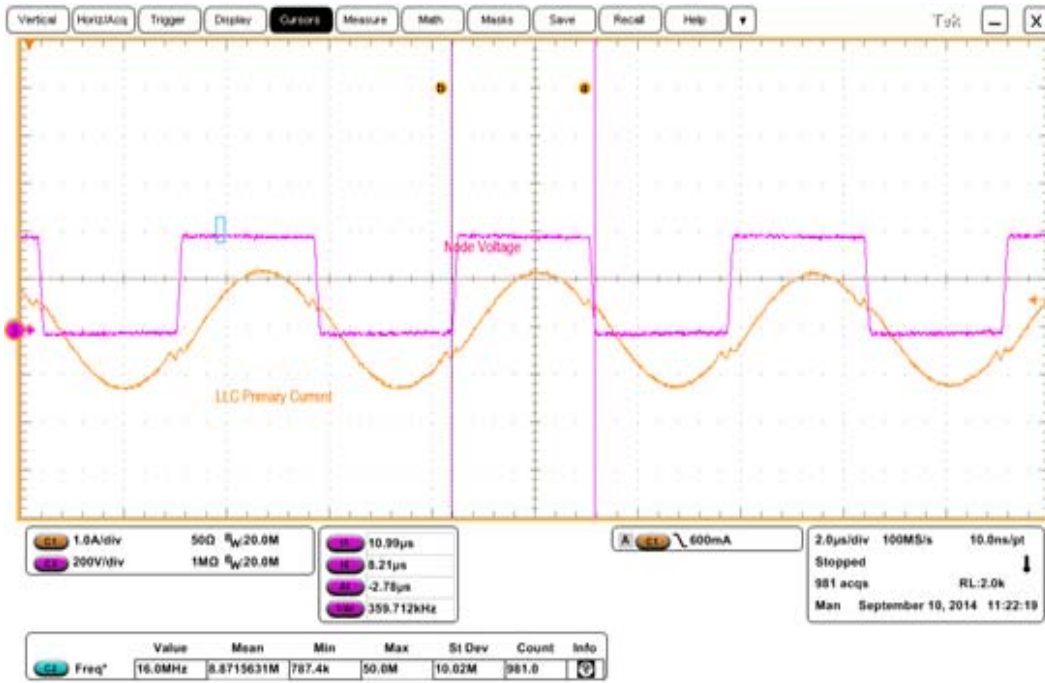


Figure 10 LLC inductor current vs node voltage (10 A load)

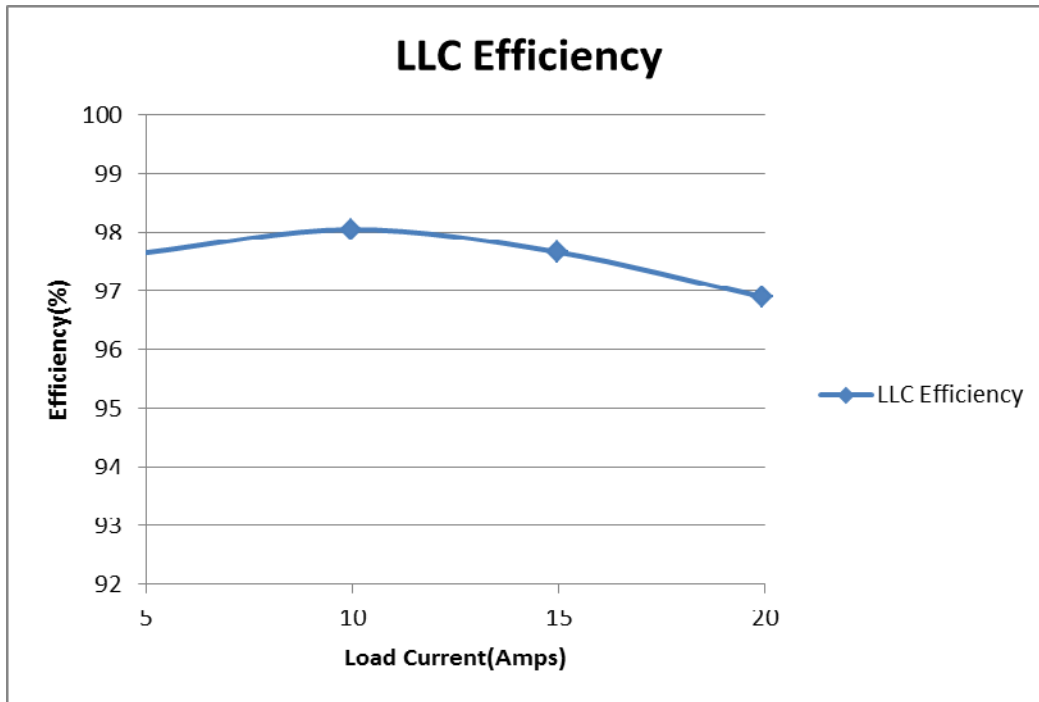


Figure 11 LLC Converter Efficiency

Board Efficiency


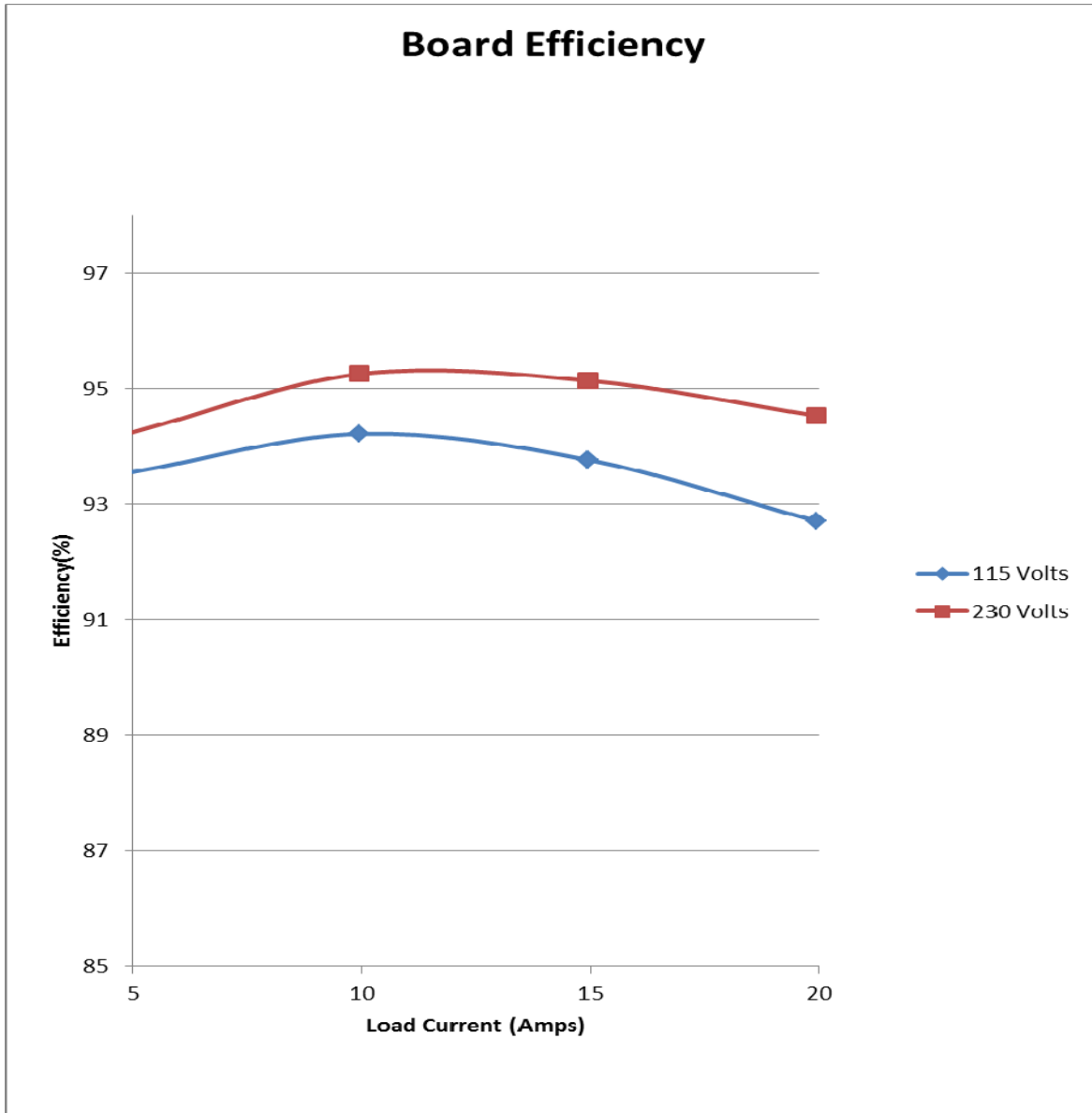


Figure 12 Complete Board Efficiency

EMI Performance

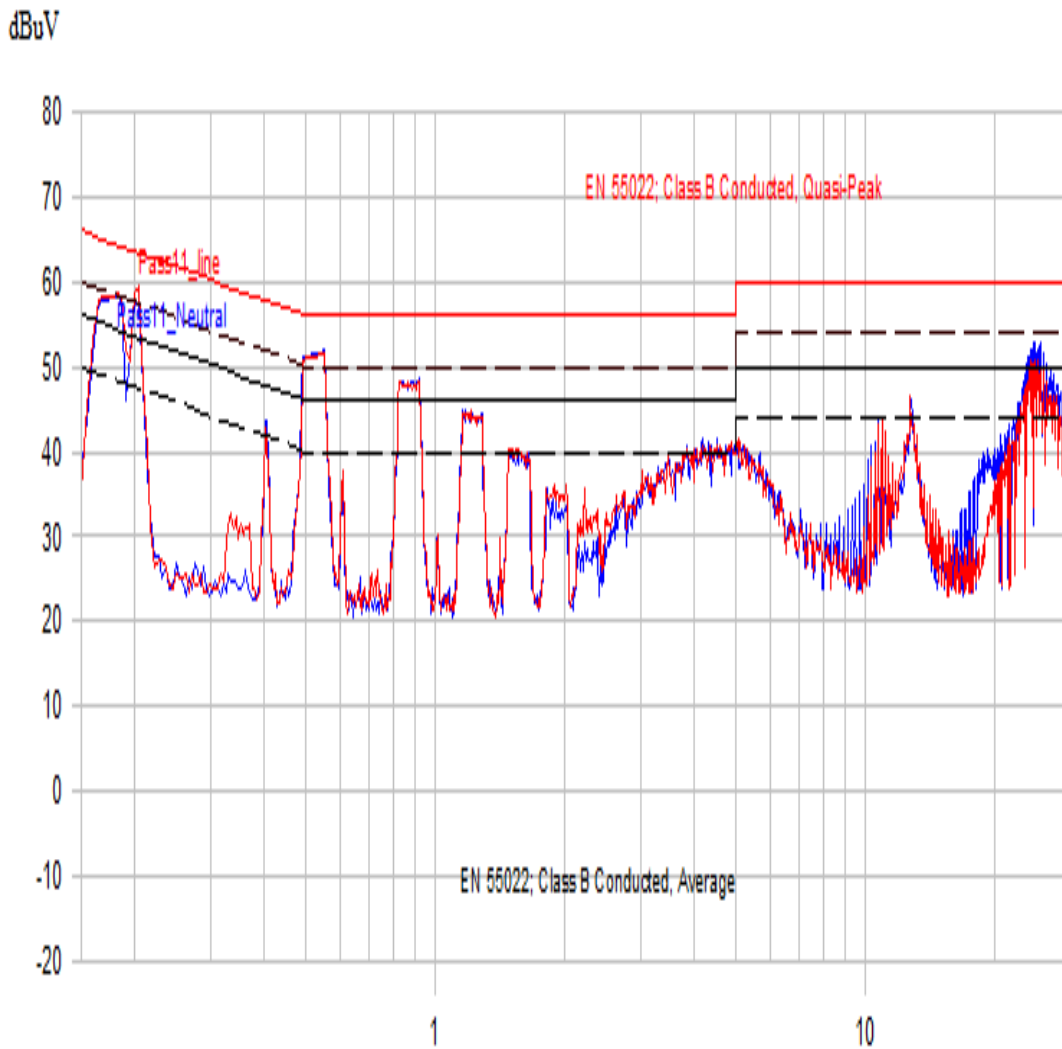EMI performance of the board was measured using spectrum analyzer and LISN. The board passes EN55022B standard. The results are shown below



8/18/2014 6:31:32 PM

(Start = 0.15, Stop = 30.00) MHz

Figure 13 Conducted Emission results as per EN55022

Surge Test

The board passed surge test at 2.2 kV at common mode and 1.1 kV differential mode settings.

Complete Schematic

Complete schematic of the board is shown in the figures below.


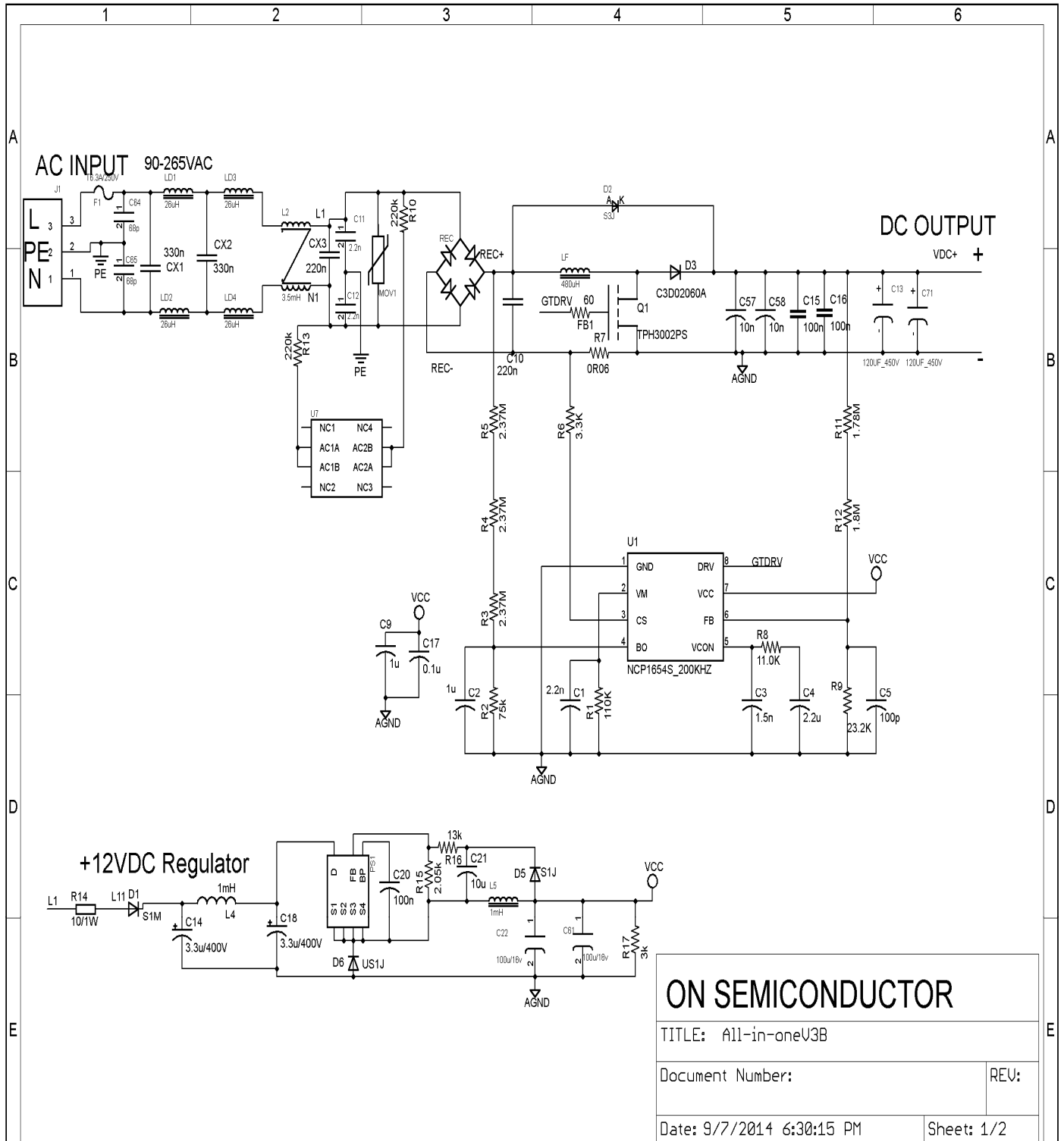


Figure 14 Complete schematic page 1

DN05067/D

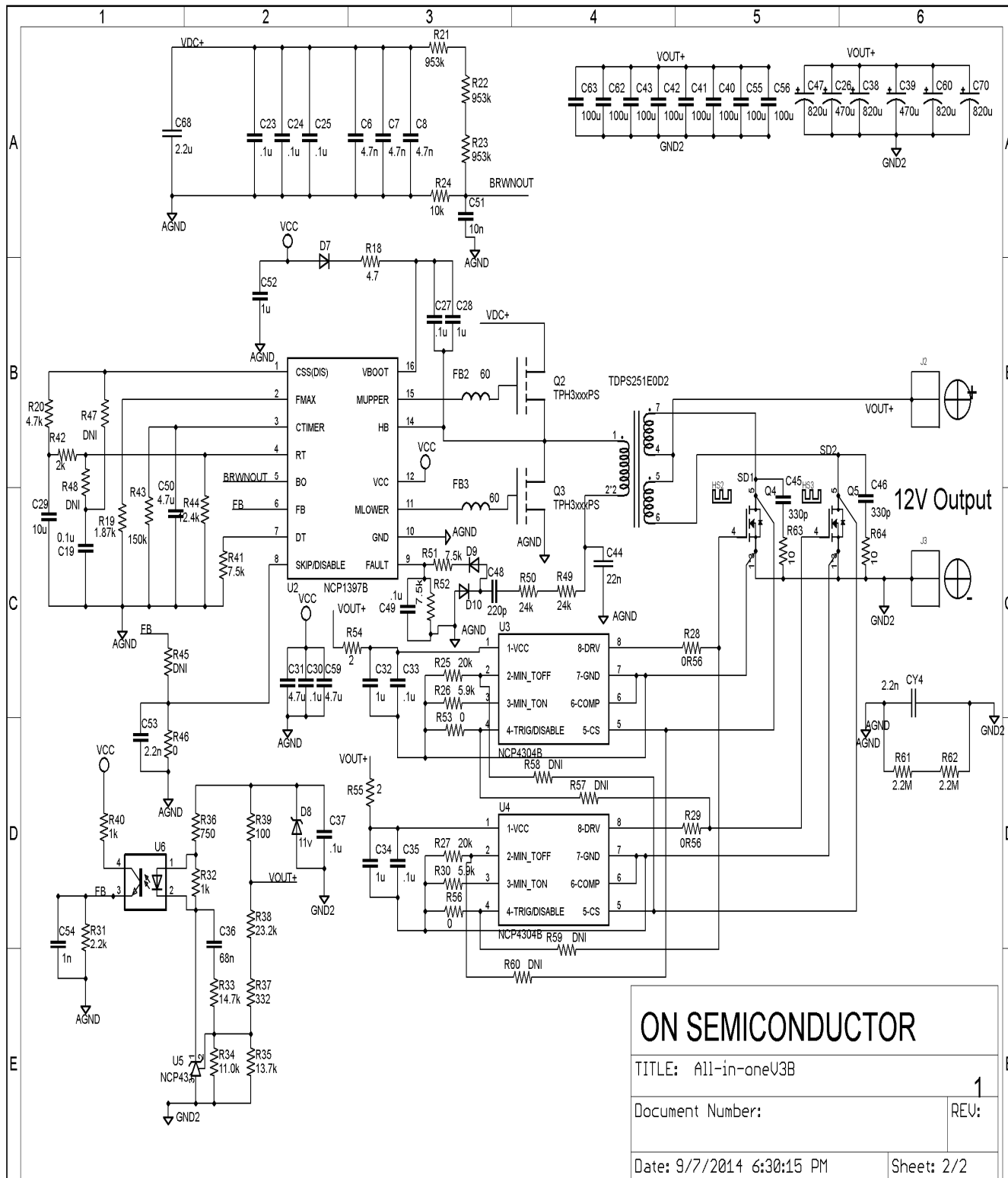

| | |
|---------------------------|------------|
| ON SEMICONDUCTOR | |
| TITLE: All-in-oneV3B | |
| Document Number: | 1 |
| Date: 9/7/2014 6:30:15 PM | Sheet: 2/2 |

Figure 15 Complete schematic page 2

Bill of Material

| Items | Qty | Reference | Part Description | Manufacture, Part No. |
|-------|-----|--|---|----------------------------------|
| 1 | 2 | C1, C53 | CAP., X7R, 2.2nF, 16V, 10%, 0603 | AVX, 0603YC222KAT2A |
| 2 | 6 | C2, C9, C28, C32, C34, C52 | CAP., X7R, 1μF, 16V, 10%, 0603 | Taiyo Yuden, EMK107B7105KA-T |
| 3 | 1 | C3 | CAP., X7R, 1.5nF, 16V, 10%, 0603 | Kemet, C0603C152K4RACTU |
| 4 | 1 | C4 | CAP., X5R, 2.2μF, 16V, 10%, 0603 | TDK, C1608X5R1C225K080AB |
| 5 | 1 | C5 | CAP., NP0, 100pF, 50V, 5%, 0603 | AVX, C1608C0G1H101J080AA |
| 6 | 3 | C6, C7, C8 | CAP., NP0, 4.7nF, 630V, 5%, 1206 | TDK, C3216C0G2J472J085AA |
| 7 | 2 | C10 | CAP., Film, 0.22μF, 630V, 20%, 7x15x17.5(mm) | Vishay, BFC233820224 |
| 8 | 3 | CY1, CY2, CY4 | CAP., X1Y2, 4.7nF, 250VAC, 20%, Rad. | Kemet, C947U472MYVDBA7317 |
| 9 | 2 | C13, C71 | CAP., Alum., 120μF, 450V, 20%, Rad. 18x33.5(mm) | Rubycon, 450QXW120MEFC18X31.5 |
| 10 | 2 | C14, C18 | CAP., Alum., 3.3μF, 400V, 20%, E3.5-8 | Rubycon, 400LLE3R3MEFC8X11R5 |
| 11 | 5 | C15, C16, C23, C24, C25 | CAP., X7R, 0.1μF, 630V, 10%, 1812 | TDK, C4532X7R2J104K230KA |
| 12 | 7 | C17, C19, C27, C30, C33, C35, C37 | CAP., X7R, 0.1μF, 25V, 10%, 0603 | Kemet, C0603C104K3RACTU |
| 13 | 1 | C20 | CAP., X7R, 0.1μF, 25V, 10%, 1206 | Kemet, C1206F104K3RACTU |
| 14 | 2 | C21, C29 | CAP., X5R, 10μF, 16V, 20%, 0805 | Kemet, C0805C106M4PACTU |
| 15 | 2 | C22, C61 | CAP., Alum., 100μF, 16V, 20%, Rad. 5x2(mm) | Rubycon, 16PX100MEFCTA5X11 |
| 16 | 1 | C26 | CAP., Poly. Alum., 470μF, 16V, 20%, E3.5-8 | Nichicon, PLG1C471MDO1 |
| 17 | 3 | C31, C50, C59 | CAP., X5R, 4.7μF, 16V, 10%, 0805 | Kemet, C0805C475K4PACTU |
| 18 | 1 | C36 | CAP., X7R, 68nF, 16V, 10%, 0603 | Yageo, CC0603KRX7R7BB683 |
| 19 | 3 | C38, C47, C70 | CAP., Alum., 820μF, 16V, 20%, E5-10.5 | Panasonic, EEU-FC1C821 |
| 20 | 1 | C39 | CAP., Alum., 680μF, 16V, 20%, E3.5-8 | Panasonic, EEU-FC1C681L |
| 21 | 8 | C40, C41, C42, C43, C55, C56, C62, C63 | CAP., X5R, 100μF, 16V, 20%, 1210 | Taiyo Yuden, EMK325ABJ107MM-T |
| 22 | 1 | C44 | CAP., Film, 22nF, 1kV, 5%, 26x6.5(mm) | Kemet, PHE450PD5220JR06L2 |
| 23 | 2 | C45, C46 | CAP., NP0, 330pF, 50V, 5%, 0805 | Kemet, C0805C331J5GACTU |
| 24 | 1 | C51 | CAP., X7R, 10nF, 16V, 10%, 0603 | TDK, CGJ3E2X7R1C103K080AA |
| 25 | 1 | C54 | CAP., X7R, 1nF, 16V, 5%, 0603 | Kemet, C0603C102J4RACTU |
| 26 | 2 | C57, C58 | CAP., NP0, 10nF, 630V, 5%, 1206 | TDK, C3216C0G2J103J160AA |
| 27 | 2 | CX1, CX2 | CAP., Film, 0.47 μF, 630VDC, 20%, 10x16.5x17.5(mm) | Vishay, BFC233920474 |
| 28 | 1 | C60 | CAP., Poly. Alum., 820μF, 16V, 20%, E5-10.5 | Nichicon, PLG1C821MDO1 |
| 29 | 1 | C68 | CAP., Flim, 2.2μF, 450V, 5%, 18.8x12.8(mm) | Panasonic, ECW-F2W225JA |
| 30 | 1 | R1 | RES., 110k, 0.1W, 1%, 0603 | Vishay, CRCW0603110KFKEA |
| 31 | 1 | R2 | RES., 75k, 0.1W, 5%, 0603 | Vishay, CRCW060375K0JNEA |
| 32 | 3 | R3, R4, R5 | RES., 2.37M, 1/8W, 1%, 0805 | Yageo, RC0805FR-072M37L |
| 33 | 2 | R6, R19 | RES., 3.3k, 0.1W, 1%, 0603 | Stackpole, RMCF0603FT3K30 |
| 34 | 1 | R7 | RES., 60mΩ, 1W, 1%, 2512 | Vishay, WSL2512R0600FEA |
| 35 | 2 | R8, R34 | RES., 11k, 0.1W, 1%, 0603 | Panasonic, ERJ-3EKF1102V |

DN05067/D

| | | | | |
|----|---|------------------------------|--|---------------------------------|
| 36 | 2 | R9, R38 | RES., 23.2k, 0.1W, 1%, 0603 | Panasonic, ERA-3AEB2322V |
| 37 | 2 | R10, R13 | RES., 220k, 1/4W, 1%, 1206 | Yageo, RC1206FR-07220KL |
| 38 | 1 | R11 | RES., 1.8M, 1/8W, 1%, 0805 | Rohm, KTR10EZPF1804 |
| 39 | 1 | R12 | RES., 1.78M, 1/8W, 1%, 0805 | Vishay, CRCW08051M78FKEA |
| 40 | 1 | R14 | RES., 10 Ω , 1W, 1%, 2010 | Stackpole, RMCP2010FT10R0 |
| 41 | 1 | R15 | RES., 2.05k, 0.1W, 1%, 0603 | Yageo, RC0603FR-072K05L |
| 42 | 1 | R16 | RES., 13k, 0.1W, 1%, 0603 | Yageo, RC0603FR-0713KL |
| 43 | 1 | R17 | RES., 13k, 1/4W, 5%, 1206 | Panasonic, ERJ-8GEYJ133V |
| 44 | 1 | R18 | RES., 4.7 Ω , 1/8W, 1%, 0805 | Rohm, KTR10EZPF4R70 |
| 45 | 1 | R20 | RES., 4.7k, 0.1W, 1%, 0603 | Rohm, MCR03ERTF4701 |
| 46 | 3 | R21, R22, R23 | RES., 953k, 1/8W, 1%, 0603 | Panasonic, ERJ-6ENF9533V |
| 47 | 1 | R24 | RES., 10k, 1/8W, 1%, 0805 | Panasonic, ERJ-6ENF1002V |
| 48 | 2 | R25, R27 | RES., 20k, 0.1W, 1%, 0603 | Rohm, MCR03ERTF2002 |
| 49 | 2 | R26, R30 | RES., 5.9k, 0.1W, 1%, 0603 | Yageo, RC0603FR-075K9L |
| 50 | 2 | R28, R29 | RES., 0.56 Ω , 1/8W, 1%, 0805 | Yageo, RL0805FR-070R56L |
| 51 | 1 | R31 | RES., 2.2k, 0.1W, 1%, 0603 | Yageo, RC0603FR-072K2L |
| 52 | 3 | R32, R40, R46 | RES., 1k, 0.1W, 1%, 0603 | Yageo, RC0603FR-071KL |
| 53 | 1 | R33 | RES., 14.7k, 0.1W, 1%, 0603 | Panasonic, ERJ-3EKF1472V |
| 54 | 1 | R35 | RES., 13.7k, 0.1W, 1%, 0603 | Panasonic, ERJ-3EKF1372V |
| 55 | 1 | R36 | RES., 750 Ω , 0.1W, 1%, 0603 | Yageo, RC0603FR-07750RL |
| 56 | 1 | R37 | RES., 332 Ω , 0.1W, 1%, 0603 | Vishay, CRCW0603332RFKEA |
| 57 | 1 | R39 | RES., 100 Ω , 0.1W, 1%, 0603 | Yageo, RC0603FR-07100RL |
| 58 | 1 | R41 | RES., 7.5k, 0.1W, 1%, 0603 | Yageo, MCR03ERTF7501 |
| 59 | 1 | R42 | RES., 2k, 0.1W, 1%, 0603 | Panasonic, ERJ-3EKF2001V |
| 60 | 1 | R43 | RES., 150k, 0.1W, 1%, 0603 | Yageo, RC0603FR-07150KL |
| 61 | 1 | R44 | RES., 12.4k, 0.1W, 1%, 0603 | Yageo, RC0603FR-0712K4L |
| 62 | 6 | R47, R48, R57, R58, R59, R60 | RES., N/A, 0603 | N/A |
| 63 | 1 | R45 | RES., 6.8k, 0.1W, 1%, 0603 | Yageo, RC0603FR-076K8L |
| 64 | 3 | R53, R56, R52 | RES., 0 Ω , 0.1W, 0603 | Yageo, RC0603JR-070RL |
| 65 | 2 | R49, R50 | RES., 24k, 1/8W, 5%, 0805 | Yageo, RC0805JR-0724KL |
| 66 | 2 | R54, R55 | RES., 4.7 Ω , 0.1W, 1%, 0603 | Panasonic, P4.7AJCT-ND |
| 67 | 2 | R61, R62 | RES., 2.2M, 1/4W, 5%, 1206 | Yageo, RC1206JR-072M2L |
| 68 | 2 | R63, R64 | RES., 10 Ω , 1/4W, 5%, 0805 | Stackpole, RPC0805JT10R0 |
| 69 | 1 | D1 | Diode, 1000V, 1A, DO-214AC | Diode Inc, S1M-13-F |
| 70 | 1 | D2 | Diode, 600V, 3A, DO-214AB | Fairchild, S3J |
| 71 | 1 | D3 | Diode, SiC, 600V, 2A, TO220-2 | Cree, C3D02060A |
| 72 | 1 | D5 | Diode, 600V, 1A, DO-214AC | Diode Inc, S1J-13-F |
| 73 | 1 | D6 | Diode, Ultra Fast, 600V, 1A, DO-214AC | Diode Inc, US1J-13-F |
| 74 | 1 | D7 | Diode, Ultra Fast, 600V, 1A, DO-214AC | Micro Commercial Inc., ES1J-LTP |
| 75 | 1 | D8 | Diode, Zener, 11V, 0.5W, SOD123 | On-Semi., MMSZ5241BT1G |
| 76 | 2 | D9, D10 | Diode, 75V, 0.15A, SOD323F | Fairchild, 1N4148WS |
| 77 | 3 | Q1, Q2, Q3 | GaN HEMT, 600V, 9A, TO220 | Transphorm, TPH3002PS |
| 78 | 2 | Ld1, Ld2 | IND., 90 μ H, DCR<40m Ω | Würth Elek., 7447013 |
| 79 | 1 | L3 | Common Mode Chk, 10mH, 1.9A, 22x15(mm) | Würth Elek., 744 824 310 |
| 80 | 1 | L4 | IND., 1mH, 70mA, 1812 | Würth Elek., 744045102 |
| 81 | 2 | Ld3, Ld4 | Shorted | N/A |

DN05067/D

| | | | | |
|-----|---|---------------|---|-----------------------------|
| 82 | 1 | L5 | IND., 1mH, 0.235A, 7.6x7.6(mm) | Cooper Buss., DRA73-102-R |
| 83 | 1 | LF | IND., 480μH, 200kHz, CC30/19 | Precision, 019-8202-00R |
| 84 | 1 | J1 | CONN., 300V, 10A, 3Pin_3.5mm | Würth Elek., 691214110003 |
| 85 | 2 | J2, J3 | BUSH, 54A | Würth Elek., 7461093 |
| 86 | 2 | HS2, HS3 | HEATSINK, 10x10(mm) | Assmann WSW Comp., V2017B |
| 87 | 1 | PS1 | PowerChip, Offline, 12V, 1.44W, SO-8C | Power Integ., LNK304DG-TL |
| 88 | 1 | MOV1 | MOV, 504V, 3.5kA, Disc 10.5mm | Panasonic, ERZ-E08A561 |
| 89 | 1 | U2 | LLC Controller, 16-SOIC | On-Semi, NCP1397BDR2G |
| 90 | 1 | U1 | PFC Controller, CCM, 200kHz, SO-08 | On-Semi, NCP1654BD200R2G |
| 91 | 2 | U3,U4 | Synchronous Rectifier Driver, SO-08 | On-Semi, NCP4304BDR2G |
| 92 | 1 | U5 | Voltage Reference, SOT23 | On-Semi, NCP432BCSNT1G |
| 93 | 1 | U6 | Optoisolator, 5kV, 4-SMD | Avargo, HCPL-817-50AE |
| 94 | 1 | U7 | X2 CAP. DIS., SOIC-8 | On-Semi, NCP4810DR2G |
| 95 | 1 | F1 | FUSE, SLOW, 250V, 6.3A | Littlefuse Inc, 39216300000 |
| 96 | 2 | Q4, Q5 | MOSFET, N-CH, 40V, 100A, PG-TDSON-8 | Infineon, BSC017N04NS G |
| 97 | 1 | Transformer | Transformer, LLC, 240W, 170kHz – 200kHz | Precision, 019-7896-00R |
| 98 | 3 | FB1, FB2, FB3 | Ferrite Bead, 60Ω@100MHz, 500mA, 0603 | TDK, MMZ1608Y600B |
| 99 | 1 | REC | Rectifier Bridge, 600V, 8A, D-72 | Vishay, VS-KBPC806PBF |
| 100 | 1 | N/A | Thermal Pad, 0.9W/m-K, 18.42x13.21(mm) | Aavid Thermalloy, 53-77-9G |
| 101 | 1 | N/A | Ferrite Core, 47Ω@100MHz, 4.2mm OD | Würth Elek., 74270012 |
| | | | | |
| | | | | |

Table 5 Bill of Material

Startup sequence:

1. Connect a load. The load should be resistive, and maximum of 240watt at 12Vdc;
2. Connect an AC power source, set to the desired voltage higher than 90V.
3. Place a cooling fan facing the GaN HEMTs heat sink of PFC (provide a minimum of 30 CFM air flow).
4. Turn on the cooling fan if output power is higher than 155W (>70% Load);

Probing Instructions:

In order to minimize additional inductance during measurement, the tip and the ground of the probe should be directly attached to the sensing points to minimize the sensing loop; while the typical long ground lead should be avoided since it will form a sensing loop and could pick up the noise. The differential probes are not recommended for the GaN signal measurement.

References:

- [1]. Datasheet of NCP1654, website: www.onsemi.com, On Semiconductor.
- [2]. Datasheet of NCP1397, website: www.onsemi.com, On Semiconductor.
- [3]. Datasheet of NCP4304, website: www.onsemi.com, On Semiconductor.
- [4]. AND8324-D Application Note, website: www.onsemi.com, On Semiconductor.
- [5]. Bo Yang, F.C. Lee, A.J. Zhang, H. Guisong, "LLC resonant converter for front end DC/DC conversion" *Proc. IEEE APEC'02*, pp.1108 – 1112, 2002.
- [6]. Application Note. TDPS250E2D2 All in One Power Supply, website: www.transphormusa.com, Transphorm Inc.
- [7] Datasheet of TPH3002PS, website www.transphorm.com

© 2014 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

DN05067/D

Design note created by Tim Kaske, e-mail: Tim.Kaske@onsemi.com



Компания «ЭлектроПласт» предлагает заключение долгосрочных отношений при поставках импортных электронных компонентов на взаимовыгодных условиях!

Наши преимущества:

- Оперативные поставки широкого спектра электронных компонентов отечественного и импортного производства напрямую от производителей и с крупнейших мировых складов;
- Поставка более 17-ти миллионов наименований электронных компонентов;
- Поставка сложных, дефицитных, либо снятых с производства позиций;
- Оперативные сроки поставки под заказ (от 5 рабочих дней);
- Экспресс доставка в любую точку России;
- Техническая поддержка проекта, помощь в подборе аналогов, поставка прототипов;
- Система менеджмента качества сертифицирована по Международному стандарту ISO 9001;
- Лицензия ФСБ на осуществление работ с использованием сведений, составляющих государственную тайну;
- Поставка специализированных компонентов (Xilinx, Altera, Analog Devices, Intersil, Interpoint, Microsemi, Aeroflex, Peregrine, Syfer, Eurofarad, Texas Instrument, Miteq, Cobham, E2V, MA-COM, Hittite, Mini-Circuits, General Dynamics и др.);

Помимо этого, одним из направлений компании «ЭлектроПласт» является направление «Источники питания». Мы предлагаем Вам помощь Конструкторского отдела:

- Подбор оптимального решения, техническое обоснование при выборе компонента;
- Подбор аналогов;
- Консультации по применению компонента;
- Поставка образцов и прототипов;
- Техническая поддержка проекта;
- Защита от снятия компонента с производства.



Как с нами связаться

Телефон: 8 (812) 309 58 32 (многоканальный)

Факс: 8 (812) 320-02-42

Электронная почта: org@eplast1.ru

Адрес: 198099, г. Санкт-Петербург, ул. Калинина, дом 2, корпус 4, литера А.